

CHAPTER 7

7.1 (a) $16\text{ K} \times 8 \Rightarrow$ Address lines = 14, Data lines = 8

(b) $512\text{ K} \times 16 \Rightarrow$ Address lines = 19, Data lines = 16

(c) $32\text{ M} \times 32 \Rightarrow$ Address lines = 25, Data lines = 32

(d) $8\text{ G} \times 16 \Rightarrow$ Address lines = 33, Data lines = 16

7.2 (a) 16 K Bytes

(b) 1024 K Bytes

(c) 128 M Bytes


(d) 16 G Bytes

7.3 1024×16 memory \Rightarrow Address line = 10, Data line = 16

word: no. 875 \Rightarrow Address bits = 11011011011

data 46654 \Rightarrow 16-bit data = 1011 0110 0011 1110
= B63E₁₆

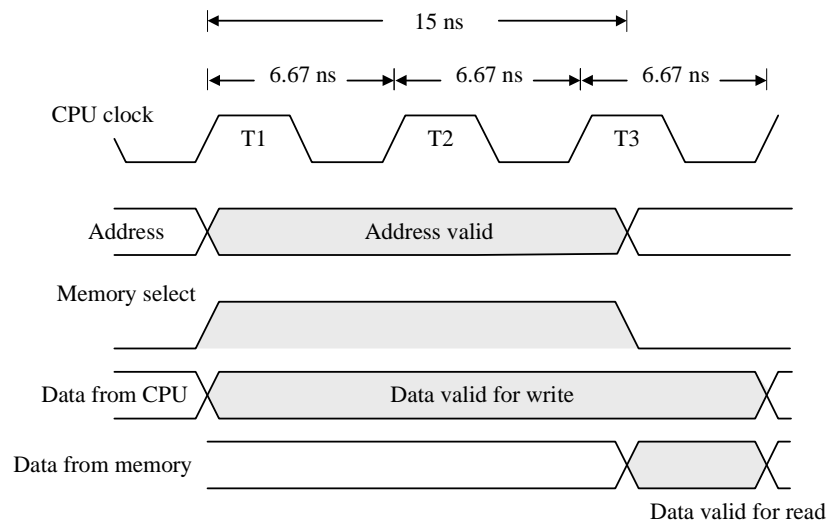
7.4 $f_{\text{CPU}} = 150\text{ MHz}$, $T_{\text{CPU}} = 1/f_{\text{CPU}} = 6.67^{-9}\text{ Hz}^{-1}$



7.5

Pending

7.6

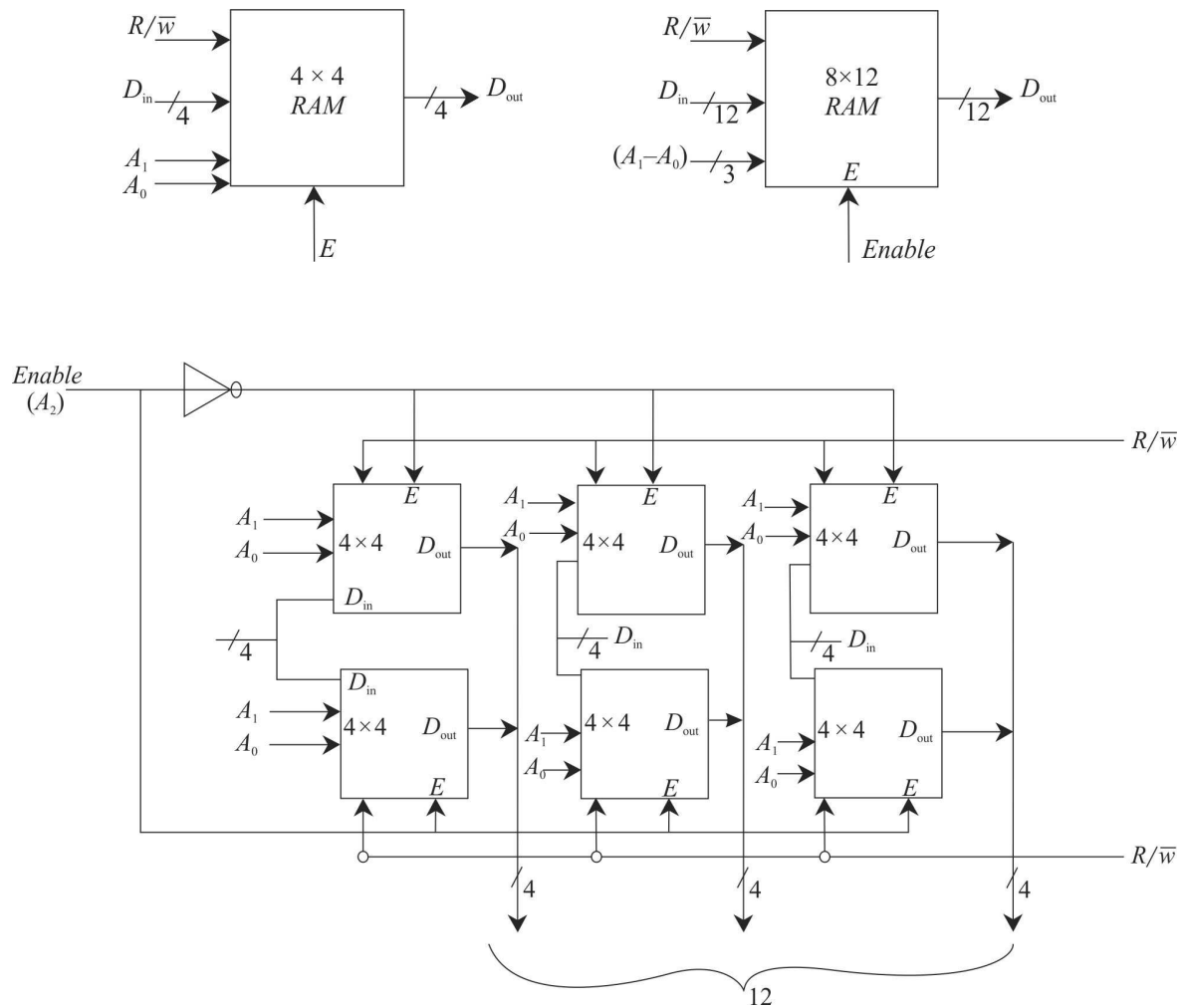

- 7.7 (a) $64\text{ K} = 2^{16} = 2^8 \times 2^8 = 256 \times 256$
 Each decoder is 8 : 256
 Decoder requires 512 AND gates, each with 8 inputs.

- (b) $36,952 = 1001\ 0000\ 0101\ 1000$
 $X = 1001\ 0000 = 144$
 $Y = 0101\ 1000 = 88$

- 7.8 (a) $\frac{512\text{ K}}{64\text{ K}} = 8$ chips
 (b) $512\text{ K} = 2^{19} \Rightarrow 19$ -bit address lines.

$64\text{ K} = 2^{16} \Rightarrow 16$ -lines are connected to each chip

and remaining $(19 - 16) = 3$ are for
 selecting the chips.

(c) $19 - 16 = 3$ lines with 3×8 decoder.

7.9 Capacity of memory = $2^{15+16} = 2^{31}$ words = 2G.

7.10 Bit position = 1 2 3 4 5 6 7 8 9 10 11 12 13 14

P_1 P_2 0 P_4 1 1 0 P_8 1 0 1 0 1 1

P_1 = XOR of (3, 5, 7, 9, 11, 13) = XOR of (0, 1, 0, 1, 1, 1) = 0

P_2 = XOR of (3, 6, 7, 10, 11, 14) = XOR of (0, 1, 0, 0, 1, 1) = 0

P_4 = XOR of (5, 6, 7, 12, 13, 14) = XOR of (1, 1, 0, 0, 1, 1) = 0

P_8 = XOR of (9, 10, 11, 12, 13, 14) = XOR of (1, 0, 1, 0, 1, 1) = 0

Composite 14-bit code word = 00 0011 0010 1011

7.11 Bit position 1 2 3 4 5 6 7 8 9 10 11 12 13

P_1 P_2 1 P_4 1 0 1 P_8 1 0 1 1 0

P_1 = XOR of (3, 5, 7, 9, 11, 13) = XOR of (1, 1, 1, 1, 1, 0) = 1

P_2 = XOR of (3, 6, 7, 10, 11) = XOR of (1, 0, 1, 0, 1) = 1

P_4 = XOR of (5, 6, 7, 12, 13) = XOR of (1, 0, 1, 1, 0) = 1

P_8 = XOR of (9, 10, 11, 12, 13) = XOR of (1, 0, 1, 1, 0) = 1

13-bit code word = 1111101110110

7.12 Bit position 1 2 3 4 5 6 7 8 9 10 11 12 13

P_1 P_2 P_4 P_8

(a) 0 1 1 1 0 0 1 0 1 0 1 0 0

9-bit data word = 100110100

(b) 1 1 1 1 0 1 0 1 0 0 0 1 1 1

9-bit data word = 101000111

(c) 1 0 1 0 1 0 0 1 1 1 0 1 0

9-bit data word = 110011010

(d) Bit position 1 2 3 4 5 6 7 8 9 10 11 12 13

1 0 1 1 1 0 1 1 1 0 1 1 0

C_1 = XOR (1, 3, 5, 7, 9, 11, 13) = XOR (1, 1, 1, 1, 1, 1, 0) = 0

C_2 = XOR (2, 3, 6, 7, 10, 11) = XOR (0, 1, 0, 1, 0, 1) = 1

C_4 = XOR (4, 5, 6, 7, 12, 13) = XOR (1, 1, 0, 1, 1, 0) = 0

C_8 = XOR (8, 9, 10, 11, 12, 13) = XOR (1, 1, 0, 1, 1, 0) = 0

$$C_8C_4C_2C_1 = 0010 \Rightarrow \text{bit 2 with error.}$$

So, 9-bit data word 110110110

(e)	Bit position	1	2	3	4	5	6	7	8	9	10	11	12	13
		0	0	0	0	1	0	0	0	1	0	1	0	1

$$C_1 = \text{XOR}(1, 3, 5, 7, 9, 11, 13) = \text{XOR}(0, 0, 1, 0, 1, 1, 1) = 0$$

$$C_2 = \text{XOR}(2, 3, 6, 7, 10, 11) = \text{XOR}(0, 0, 0, 0, 0, 1) = 1$$

$$C_4 = \text{XOR}(4, 5, 6, 7, 12, 13) = \text{XOR}(0, 1, 0, 0, 0, 1) = 0$$

$$C_8 = \text{XOR}(8, 9, 10, 11, 12, 13) = \text{XOR}(0, 1, 1, 0, 0, 1) = 0$$

$$C_8C_4C_2C_1 = 1010 \rightarrow \text{bit 10 with error.}$$

So, 9-bit data word \rightarrow 010011101

7.13 (a) 25 bits \Rightarrow Check bits $K = 5 \Rightarrow$ 6 parity bits

+1 bit

(b) 55 bits \Rightarrow Check bits $K = 6 \Rightarrow$ 7 parity bits

+1 bit

(c) 100 bits \Rightarrow Check bits $K = 7 \Rightarrow$ 8 parity bits

+1 bit

7.14	Bit position	1	2	3	4	5	6	7	8	9
	P_1	P_2	P_3	P_4	D_5	D_6	D_7	P_8	P_9	
	0	1	0	0	1	1	0	1	1	

(a) $P_1 = \text{XOR of } (3, 5, 7, 9) = \text{XOR of } (0, 1, 0, 1) = 0$

$$\begin{aligned}
 P_2 &= \text{XOR of } (3, 6, 7) &= \text{XOR of } (0, 1, 0) &= 1 \\
 P_3 &= \text{XOR of } (5, 6, 7) &= \text{XOR of } (1, 1, 0) &= 0 \\
 P_4 &= \text{XOR of } (9) &= \text{XOR of } (1) &= 1
 \end{aligned}$$

Ans: 010011011

(b)

$$\begin{aligned}
 C_1 &= \text{XOR of } (1, 3, 5, 7, 9) &= \text{XOR of } (0, 0, 1, 0, 1) &= 0 \\
 C_2 &= \text{XOR of } (2, 3, 6, 7) &= \text{XOR of } (1, 0, 1, 0) &= 0 \\
 C_4 &= \text{XOR of } (4, 5, 6, 7) &= \text{XOR of } (0, 1, 1, 0) &= 0 \\
 C_8 &= \text{XOR of } (8, 9) &= \text{XOR of } (1, 1) &= 0 \\
 C &= C_8 C_4 C_2 C_1 = 0000
 \end{aligned}$$

(c) 9-bit composite word = 010010011

$$\begin{aligned}
 C_1 &= \text{XOR of } (1, 3, 5, 7, 9) &= \text{XOR of } (0, 0, 1, 0, 1) &= 0 \\
 C_2 &= \text{XOR of } (2, 3, 6, 7) &= \text{XOR of } (1, 0, 0, 0) &= 1 \\
 C_4 &= \text{XOR of } (4, 5, 6, 7) &= \text{XOR of } (0, 1, 0, 0) &= 1 \\
 C_8 &= \text{XOR of } (8, 9) &= \text{XOR of } (1, 1) &= 0
 \end{aligned}$$

$$C_8 C_4 C_2 C_1 = 0110 \Rightarrow \text{Error in bit 6 i.e., } D_6 = 1$$

(d) Composite word : 0 1 0 0 1 1 0 1 1 P_{10}


$$P_{10} = 1.$$

$$\begin{aligned}
 C_1 &= \text{XOR of } (1, 3, 5, 7, 9) &= \text{XOR of } (1, 1, 1, 0, 1) &= 0 \\
 C_2 &= \text{XOR of } (2, 3, 6, 7, 10) &= \text{XOR of } (1, 1, 1, 0, 1) &= 0 \\
 C_4 &= \text{XOR of } (4, 5, 6, 7) &= \text{XOR of } (0, 1, 1, 0) &= 0 \\
 C_8 &= \text{XOR of } (8, 9, 10) &= \text{XOR of } (1, 1, 1) &= 1 \\
 P &= 0
 \end{aligned}$$


Error in P_1 and D_3 , so the composite word
1110110111

$$C_8 C_4 C_2 C_1 = 1000 \text{ and } P = 0 \Rightarrow \text{indicates double error.}$$

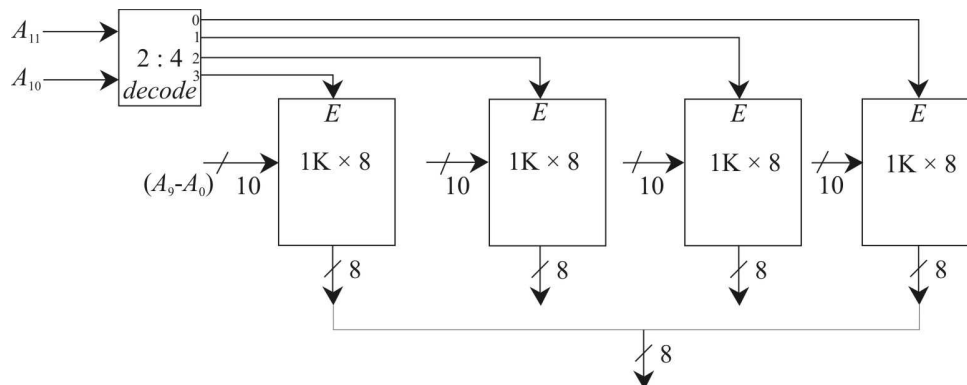7.15 To construct $4K \times 8$ ROM from $1K \times 8$ we need 4 chips.



7.16

 

$$\begin{aligned} \text{Total number of pins} &= \text{Addr line} + \text{Data line} + \text{CS} + 2 \\ &= 13 + 8 + 3 + 2 \\ &= 26 \text{ pins} \end{aligned}$$

7.17

Input Address					Output of ROM				
$I_5 I_4 I_3 I_2 I_1$	$D_6 D_5 D_4$	$D_3 D_2 D_1$	$D_0 (2^0)$	Decimal					
0 0 0 0 0	0 0 0	0 0 0	0, 1	0, 1					
0 0 0 0 1	0 0 0	0 0 1	0, 1	2, 3					
...					
...					
0 1 0 0 0	0 0 1	0 1 1	0, 1	16, 17					
0 1 0 0 1	0 0 1	1 0 0	0, 1	18, 19					
...					
...					
1 1 1 1 0	1 1 0	0 0 0	0, 1	60, 61					
1 1 1 1 1	1 1 0	0 0 1	0, 1	62, 63					

- 7.18** (a) 5-bit binary multiplier:
Size of ROM = $2^{10} \times 10 = 1K \times 10$ ROM
- (b) 5-bit adder-subtractor:
Size of ROM = $2^{11} \times 6 = 2K \times 6$ ROM

(c) Quadruple 4×1 mux:

Size of ROM = $2^{19} \times 4 = 512 \text{ K} \times 4 \text{ ROM}$

(d) 5 inputs 7 outputs $2^5 \times 7$ $32 \times 7 \text{ ROM}$

7.19

$x \backslash yz$	00	01	11	10
0	1	0	1	1
1	0	0	1	0

$$A(x, y, z) = \Sigma(0, 2, 3, 7)$$

$$= x'z' + yz$$

$$A' = xy' + xz' + y'z$$

$x \backslash yz$	00	01	11	10
0	0	1	0	1
1	1	1	0	1

$$B(x, y, z) = \Sigma(1, 2, 4, 5, 6)$$

$$A(x, y, z) = y'z + yz' + xz'$$

$x \backslash yz$	00	01	11	10
0	1	1	0	0
1	0	1	1	0

$$C(x, y, z) = \Sigma(0, 1, 5, 7)$$

$$C(x, y, z) = x'y' + xz$$

		yz			
		00	01	11	10
x	0	1	0	1	1
	1	1	0	0	1

$$D(x, y, z) = \Sigma(0, 2, 3, 4, 6)$$


$$D(x, y, z) = z' + x'y$$

$$D' = Z(x + y') = xz + y'z$$

PLA programming table:

	Product term	Inputs			Outputs			
		x	y	z	A	B	C	D
xy'	1	1	0	-	1	-	-	-
xz'	2	1	-	0	1	1	-	-
$y'z$	3	-	0	1	1	1	-	1
yz'	4	-	1	0	-	1	-	-
$x'y'$	5	0	0	-	-	-	1	-
xz	6	1	-	1	-	-	1	1
					\underline{C}	\underline{T}	\underline{T}	\underline{C}

7.20

 

Inputs				Outputs			
w	x	y	z	A	B	C	D
0	0	0	0	0	1	0	1
0	0	0	1	1	0	1	0
0	0	1	0	0	1	1	0
0	0	1	1	1	0	0	1
0	1	0	0	0	1	0	1
0	1	0	1	1	0	1	0
0	1	1	0	0	1	1	0
0	1	1	1	1	0	1	1
1	0	0	0	0	1	1	1
1	0	0	1	1	0	0	0
1	0	1	0	0	1	0	0
1	0	1	1	1	0	0	1

1	1	0	0	0	1	0	1
1	1	0	1	1	0	1	0
1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	1

7.21 Note: See truth table in Fig. 7.12(b).

		A_1A_0		A_1			
		00	01	11	10		
A_2	0	m_0 0	m_1 0	m_3 0	m_2 0		
	1	m_4 0	m_5 0	m_7 1	m_6 1	A_0	

$$F_1 = A_2A_1$$

$$F'_1 = A'_2 + A'_1$$

		A_1A_0		A_1			
		00	01	11	10		
A_2	0	m_0 0	m_1 0	m_3 0	m_2 0		
	1	m_4 1	m_5 1	m_7 1	m_6 0	A_0	

$$F_2 = A_2A'_1 + A_2A_0$$

$$F'_2 = A'_2 + A_1A'_0$$

		A_1A_0		A_1			
		00	01	11	10		
A_2	0	m_0 0	m_1 0	m_3 1	m_2 0		
	1	m_4 0	m_5 1	m_7 0	m_6 0	A_0	

$$F_3 = A'_2A_1A_0 + A_2A'_1A_0$$

$$F'_3 = A'_0 + A'_2A'_1 + A_2A_1$$

		A_1A_0		A_1			
		00	01	11	10		
A_2	0	m_0 0	m_1 0	m_3 0	m_2 1		
	1	m_4 0	m_5 0	m_7 0	m_6 1	A_0	

$$F_4 = A_1A'_0$$


$$F'_4 = A'_1 + A_0$$

Product term	Inputs $A_2A_1A_0$	Outputs			
		F_1	F_2	F_3	F_4
A_2A_1	1 1 -	1	-	-	-
A'_2	0 - -	-	1	-	-
$A_1A'_0$	- 1 0	-	1	-	1
$A'_2A_1A_0$	- 1 1	-	-	1	-
$A_2A'_1$	1 0 1	-	-	1	-
		<u>T</u>	<u>C</u>	<u>T</u>	<u>T</u>

Alternative: F'_1, F'_2, F_3, F_4
(5 terms)

7.22

Decimal	w	x	y	z	b ₇	b ₆	b ₅	b ₄	b ₃	b ₂	b ₁	b ₀	
0	0	0	0	0	0	0	0	0	0	0	0	0	
1	1	0	0	0	0	0	0	0	0	0	0	1	
2	4	0	0	1	0	0	0	0	0	1	0	0	
3	9	0	0	1	0	0	0	0	1	0	0	1	
4	16	0	1	0	0	0	0	1	0	0	0	0	
5	25	0	1	0	0	0	1	1	0	0	0	1	Note: b ₀ = z, and b ₁ = 0.
6	36	0	1	1	0	0	1	0	0	1	0	0	ROM would have 4 inputs
7	49	0	1	1	0	0	1	1	0	0	0	1	and 6 outputs. A 4 x 8
8	64	1	0	0	0	0	1	0	0	0	0	0	ROM would waste two
9	81	1	0	0	1	0	1	0	0	0	0	1	outputs.
10	100	1	0	1	0	0	1	0	0	1	0	0	
11	121	1	0	1	1	0	1	1	1	0	0	1	
12	144	1	1	0	0	1	0	0	1	0	0	0	
13	169	1	1	0	1	0	1	0	1	0	0	1	
14	196	1	1	1	0	1	1	0	0	0	1	0	
15	225	1	1	1	1	1	1	0	0	0	0	1	

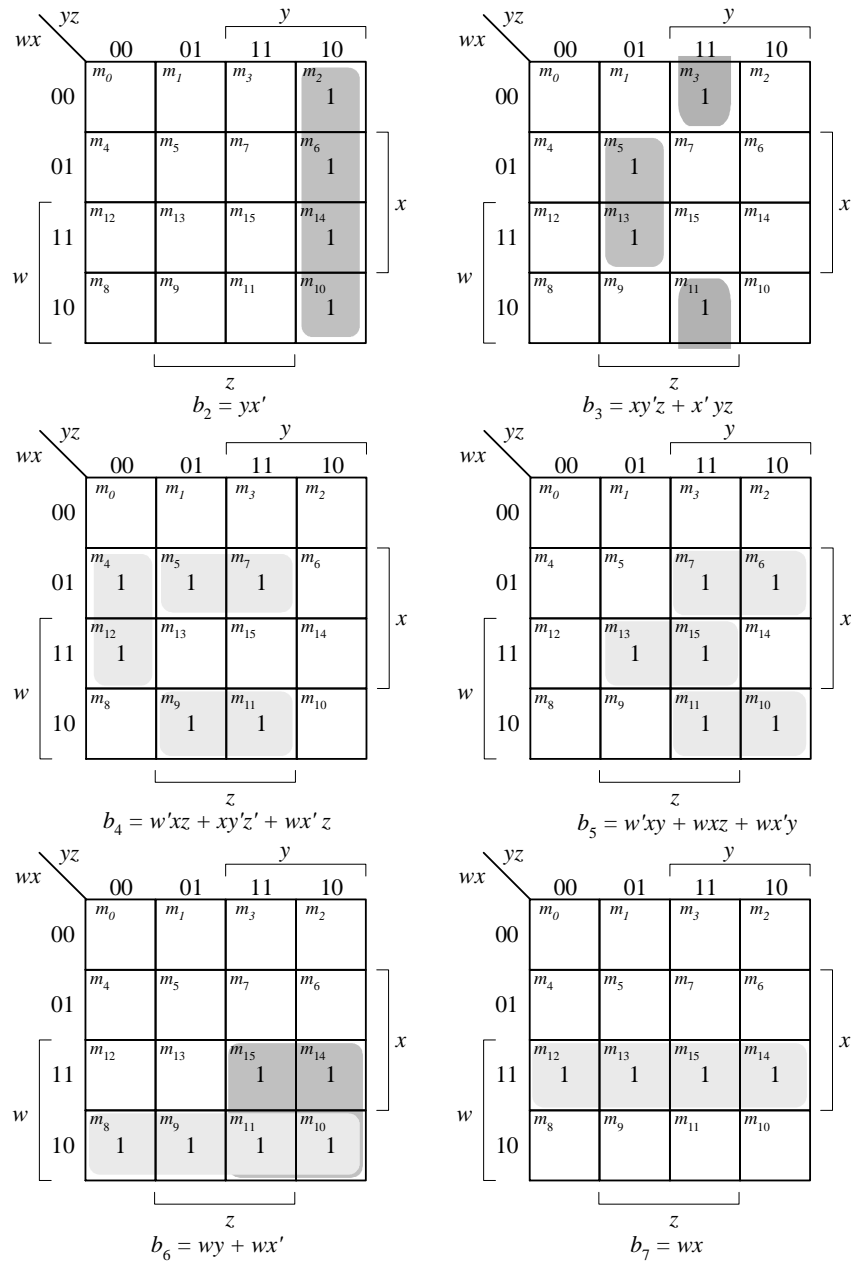

7.23

From Fig. 4-3:

$$w = A + BC + BD$$

$$w' = A'B' + A'C'D'$$

$$x = B'C + B'D + BC'D'$$

$$x' = B'C'D' + BC BD$$

$$y = CD + C'D'$$

$$y' = C'D + CD'$$

$$z = D'$$

$$z' = D$$

Use w, x', y, z (7 terms)

Product term	Inputs				Outputs			
	A	B	C	D	F_1	F_2	F_3	F_4
A	1	1	-	-	1	-	-	-
BC	2	-	1	1	1	1	-	-
BD	3	-	1	-	1	1	-	-
$B'C'D'$	4	-	0	0	0	-	1	-
CD	5	-	-	1	1	-	-	1
$C'D'$	6	-	-	0	0	-	-	1
D'	7	-	-	-	0	-	-	1
					$T \quad C \quad T \quad T$			

7.24

AND					Outputs
Product term	A	B	C	D	
1	1	-	-	-	$w = A + BC + BD$
2	-	1	1	-	
3	-	1	-	1	
4	-	0	1	-	$x = B'C + B'D + BC'D'$
5	-	0	-	1	
6	-	1	0	0	
7	-	-	1	1	$y = CD + C'D'$
8	-	-	0	0	
9	-	-	-	-	
10	-	-	-	0	$z = D'$
11	-	-	-	-	
12	-	-	-	-	

7.25

$x \backslash yz$	00	01	11	10
0	0	1	0	1
1	1	1	0	1

$$A = \Sigma(1, 2, 4, 5, 6)$$

$$A = xy' + y'z + yz'$$

$x \backslash yz$	00	01	11	10
0	0	1	0	1
1	1	1	1	1

$$B = \Sigma(1, 2, 4, 5, 6, 7)$$

$$B = x + y'z + yz'$$

$$= xy + xy' + y'z + yz'$$

$$= A + xy$$

$x \backslash yz$	00	01	11	10
0	1	0	1	1
1	1	1	1	0

$$C = \Sigma(0, 2, 3, 4, 5, 7)$$


$$C = y'z' + x'y + xz$$

$x \backslash yz$	00	01	11	10
0	0	1	1	0
1	1	1	1	0

$$D = \Sigma(1, 3, 4, 5, 7)$$

$$D = z + xy'$$


	Product term	Inputs			Outputs
		x	y	z	
xy'	1	1	0	-	$A = xy' + y'z + yz'$
$y'z$	2	-	0	1	
yz'	3	-	1	0	
A	4	-	-	-	$B = A + xy$
xy	5	1	1	-	
$y'z'$	6	-	0	0	$C = y'z' + x'y + xz$
$x'y$	7	0	1	-	
xz	8	1	-	1	
z	9	-	-	1	$D = z + xy'$
xy'	10	1	0	-	

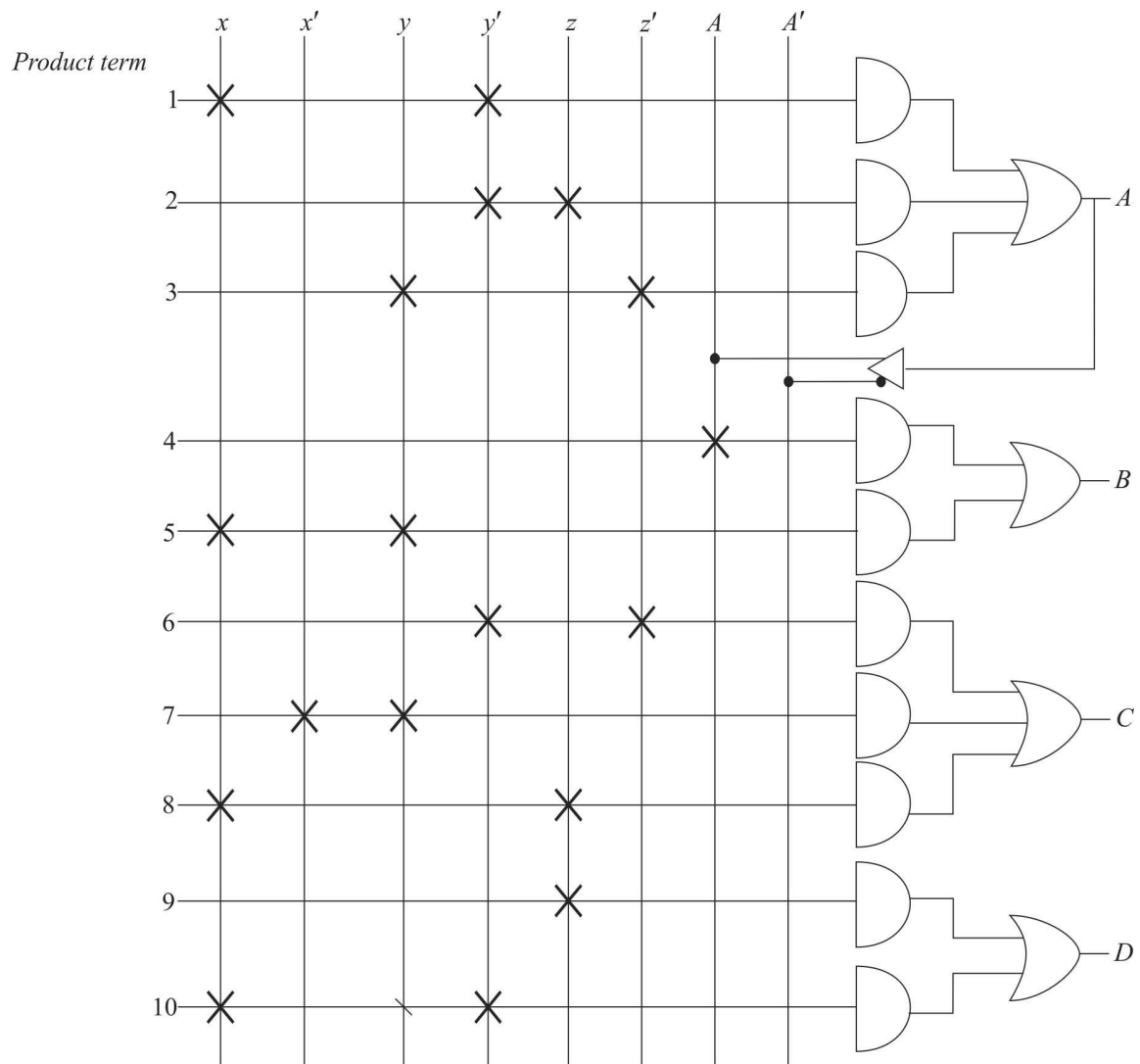

7.26 $D_A = (x \oplus y \oplus A)'$

$$= ((x \oplus y)' A' + (x \oplus y) A)$$

$$= xyA' + x'y'A' + xy'A + x'yA$$

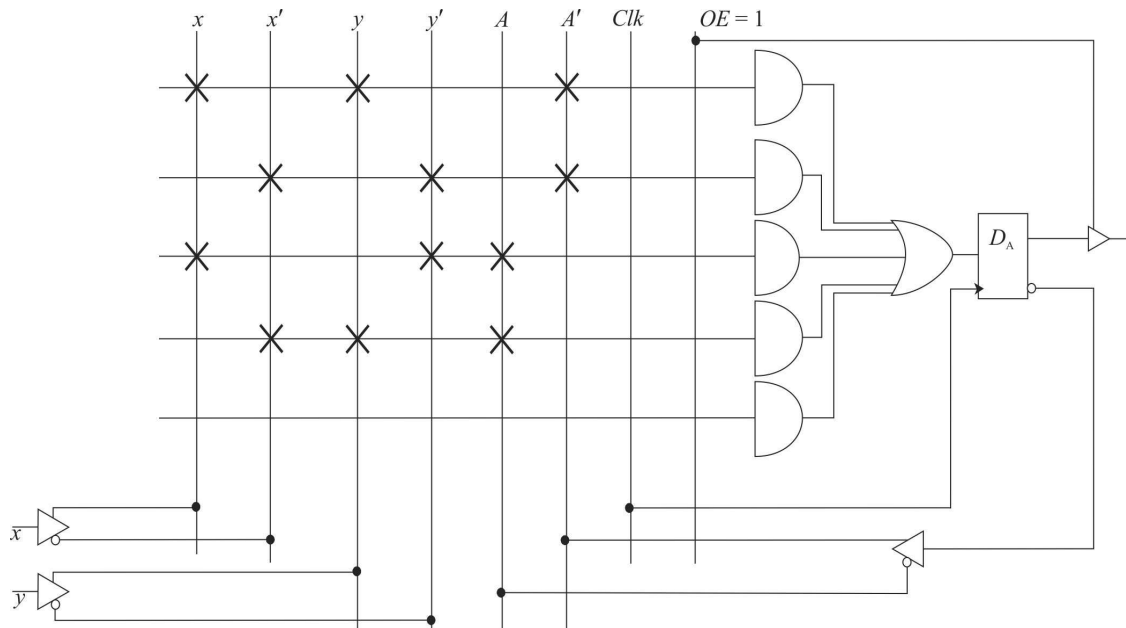

7.27


The results of Prob. 6.17 can be used to develop the equations for a three-bit binary counter with D-type flip-flops.

$$DA_0 = A'_0$$

$$DA_1 = A'_1A_0 + A_1A'_0$$

$$DA_2 = A'_2A_1A_0 + A_2A'_1 + A_2A'_0$$


$$C_{out} = A_2A_1A_0$$

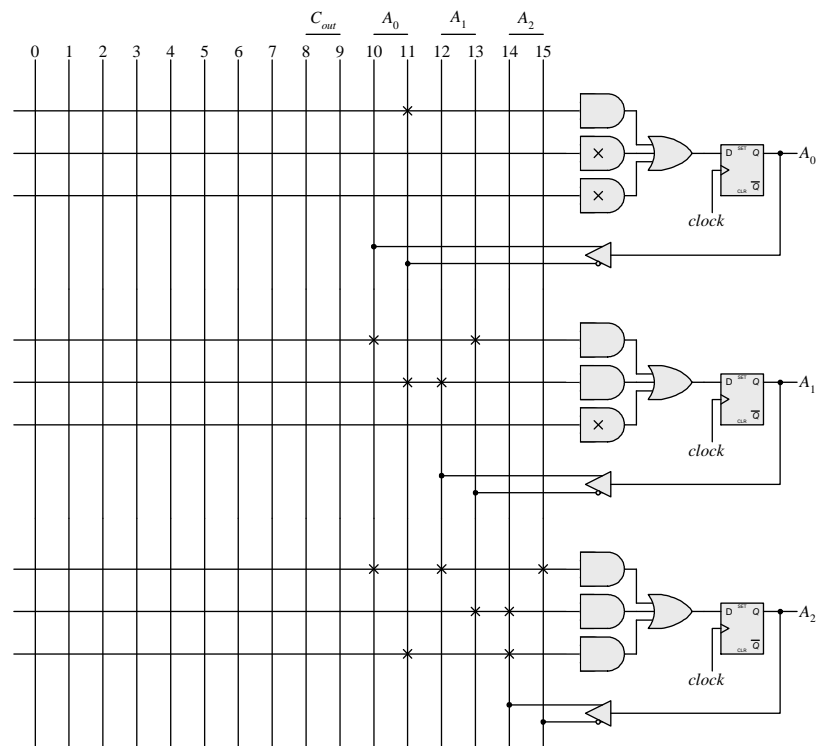

7.28

$$F_1 = AB + B'C + A'B'C'$$

$$F_2 = B'C + A'C' + ABC$$

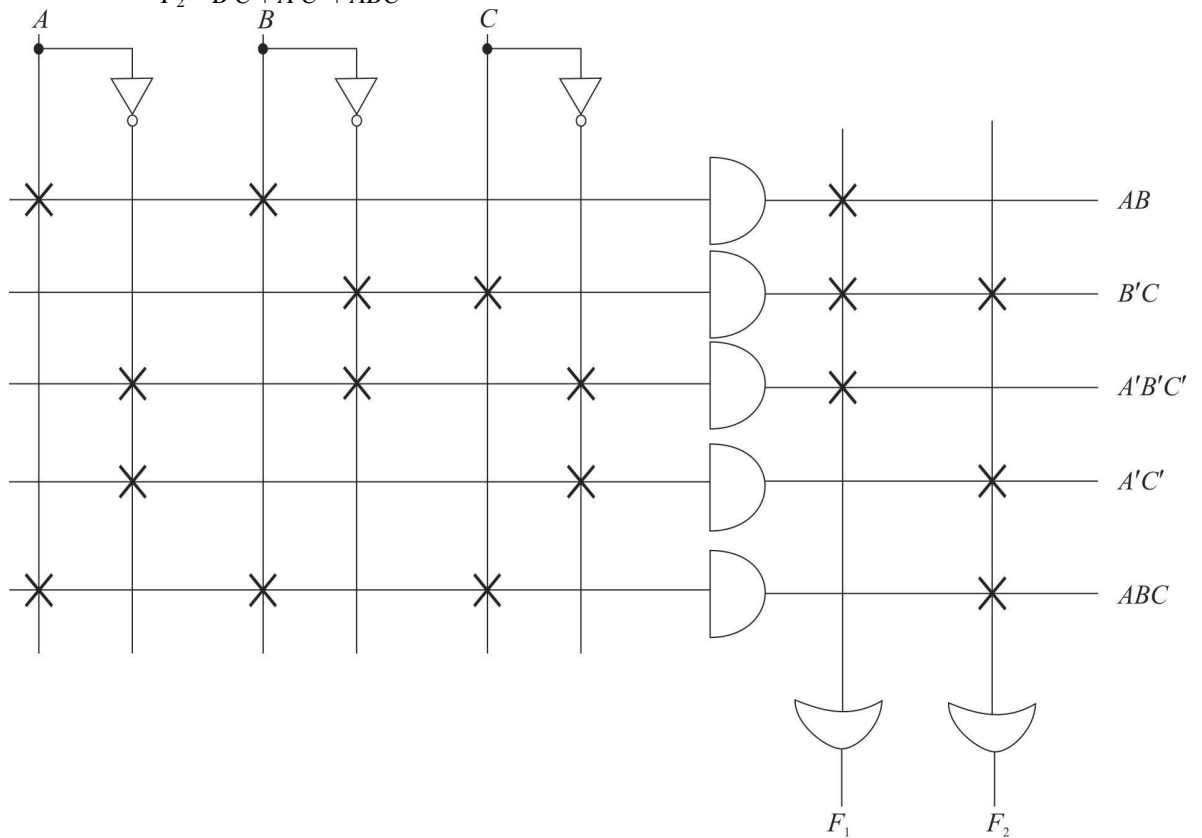

7.29 PLA programming table:

	Product term	Inputs			Outputs
		x	y	A	D_A
xyA'	1	1	1	0	1
$x'y'A'$	2	0	0	0	1
$xy'A$	3	1	0	1	1
$x'yA$	4	0	1	1	1